



www.automaticgatesolutions.com.au

HOW TO

Use E-LOOP with safety items (Eg: Photocells)

BASIC ELEMENTS -

1. E-LOOP transceiver has a normally open and common where safety inputs are generally normally closed and common.
2. Use a 12 volt relay between the transceiver and the gate logic control board to solve the issue.
3. The transceiver is powered by your logic control auxiliary power (12V DC).
4. When the transceiver switches it powers the relay which causes the normally closed relay circuit to go open.

